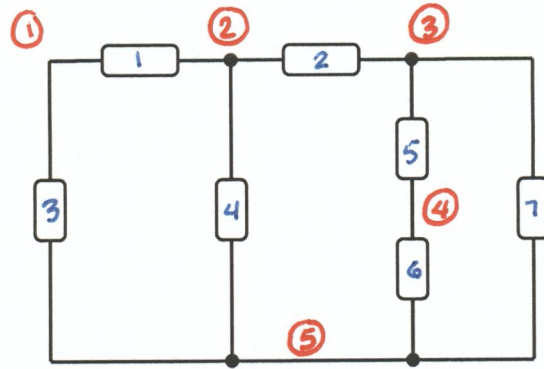


EE 2240
Problem #06



a. How many nodes does the circuit have?

5

b. How many branches does the circuit have?

7