

EE 2240
Problem #03

The $6\text{k}\Omega$ resistor is the load for this circuit. Use the method described in class to find the Norton equivalent of the remainder of the circuit. (*Why not use source transformations?*) Then determine the value of V_o .

