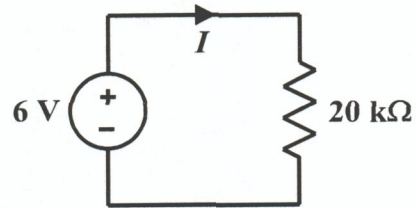


EE 2240
Problem #01

Find the current I and the power supplied by the source.



$$I = \frac{6\text{V}}{20\text{k}\Omega} = 0.3\text{ mA}$$

$$P = (6\text{V}) I = 1.8\text{ mW}$$