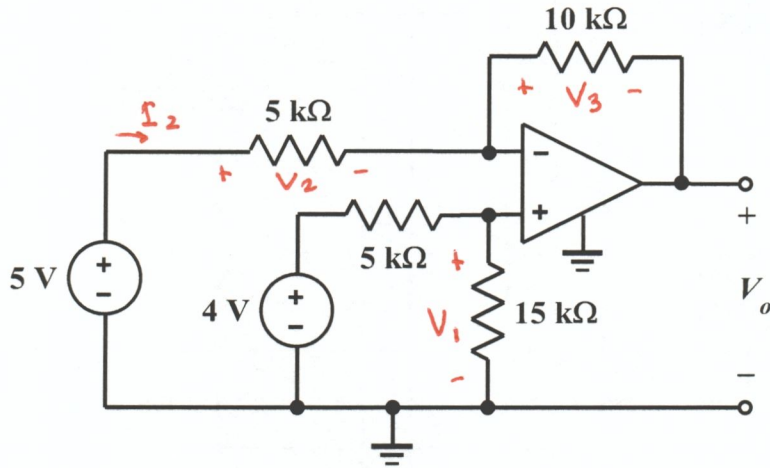


EE 2240  
Problem #07

Assume the op amp is ideal, and find  $V_o$ .



$$V_1 = \frac{15\text{k}\Omega}{5\text{k}\Omega + 15\text{k}\Omega} \cdot 4\text{V} = 3\text{V}$$

$$V_2 = 5\text{V} - V_1 = 5\text{V} - 3\text{V} = 2\text{V}$$

$$I_2 = \frac{V_2}{5\text{k}\Omega} = \frac{2\text{V}}{5\text{k}\Omega} = 400\mu\text{A}$$

$$V_3 = (10\text{k}\Omega) I_2 = (10\text{k}\Omega)(400\mu\text{A}) = 4\text{V}$$

$$V_o = -V_3 + V_1 = -4\text{V} + 3\text{V} = -1\text{V}$$