
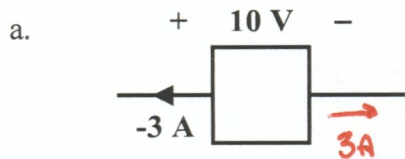


EE 2240  
Problem #01

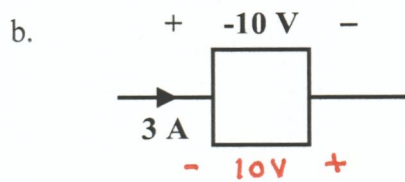
Determine whether each component *absorbs* or *delivers* power.




satisfies the PSC  
 $\Rightarrow$  absorbs power



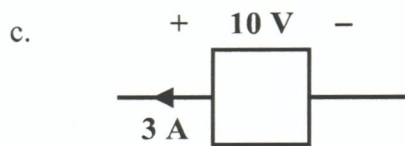
does not satisfy the PSC  
 $\Rightarrow$  delivers power



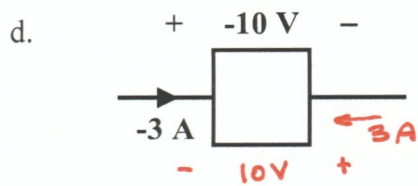does not satisfy the PSC  
 $\Rightarrow$  delivers power



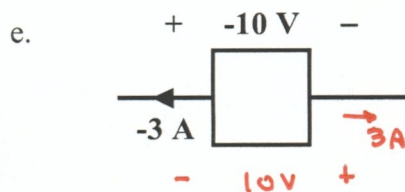satisfies the PSC  
 $\Rightarrow$  absorbs power



does not satisfy the PSC  
 $\Rightarrow$  delivers power