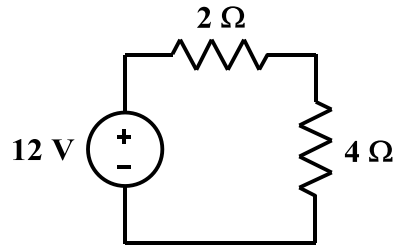


EE 2240
Problem #07

Given the circuit shown below:



- How much power does the source supply?
- How much power is absorbed by the 4Ω resistor?