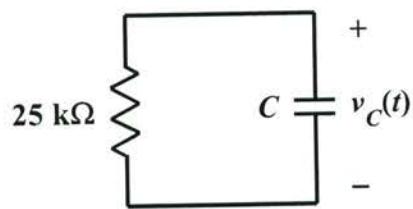


EE 2240  
**Problem #03**

The capacitor voltage,  $v_C(t)$ , in the circuit shown below is

$$v_C(t) = 5e^{-8t} \text{ V} \quad \text{for } t \geq 0.$$

Determine the value of  $C$  and the initial value of  $v_C(t)$ .



$$\frac{1}{(25\text{k}\Omega)C} = 8 \Rightarrow C = \frac{1}{8(25\text{k}\Omega)} = 5\mu\text{F}$$

$$v_C(0) = 5 \text{ V}$$