
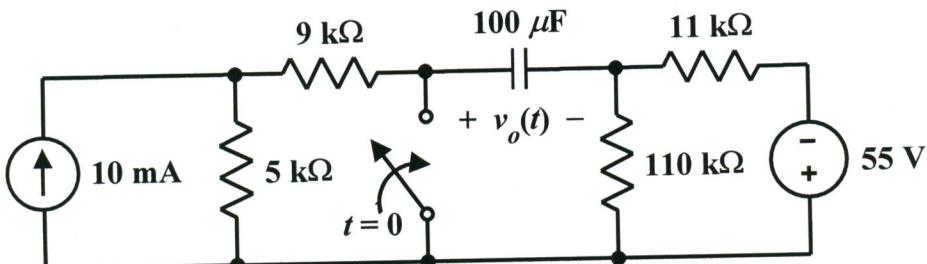


EE 2240
Problem #06

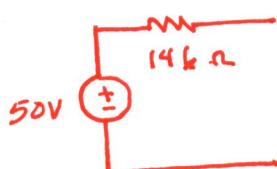
The circuit has reached the DC steady state prior to $t = 0$. Find $v_o(t)$ for $t \geq 0$.



Thévenin Eq.




Thévenin Eq.

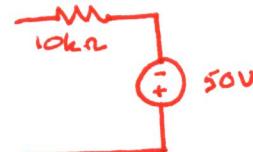

$$v_o(0) = 50 + 50 = 100 \text{ V}$$

for $t \geq 0$:

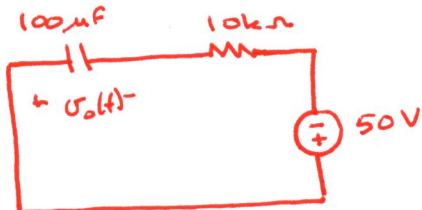

$$v_o(\infty) = 50 \text{ V}$$

$$\tau = (100 \mu\text{F})(10 \text{k}\Omega) = 1 \text{ s}$$

$$v_o(t) = [v_o(0) - v_o(\infty)] e^{-t/\tau} + v_o(\infty)$$

$$= 50 e^{-t} + 50 \quad v, t \geq 0$$