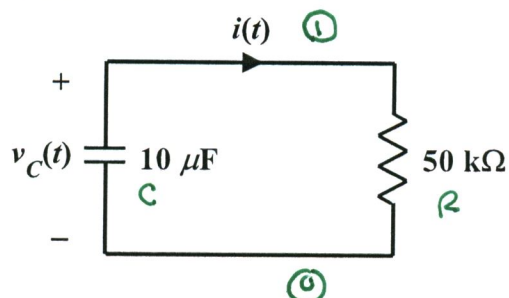


EE 2240  
**Problem #11**

Given the RC circuit shown below:



- a. Find  $v_C(t)$  for  $t \geq 0$ , if  $v_C(0) = 40$  V.

$$\tau = (50 \text{ k}\Omega)(10 \mu\text{F}) = 0.5 \text{ s}$$

$$v_C(t) = v_C(0) e^{-t/\tau}$$

$$= 40 e^{-2t} \text{ V}, t \geq 0$$

- b. Find  $i(t)$  for  $t \geq 0$ .

$$i(t) = \frac{1}{50 \text{ k}\Omega} v_C(t)$$

$$= 0.8 e^{-2t} \text{ mA}, t \geq 0$$

- c. Use PSpice and PROBE to plot the power absorbed by the resistor,  $p(t) = v_C(t) \times i(t)$ , over a time span equal to  $5 \times \tau$  where  $\tau$  is the time constant of the RC circuit.

Problem #11

```

C 1 0 10u IC=40
R 1 0 50k
.TRAN 1m 2.5 0 1m UIC
.PROBE
.END

```

↑  $5\tau = 2.5 \text{ s}$

See the next page for the output.

Problem #11

