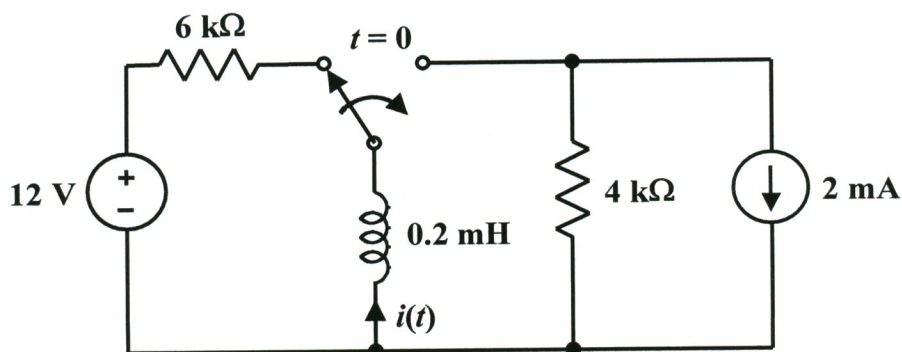


EE 2240  
**Problem #08**

Find  $i(t)$  for  $t \geq 0$  in the circuit shown and accurately sketch a plot of the response including a brief time interval just prior to switch movement.



Assuming DC steady for  $t=0^-$ ,  $i(0) = -\frac{12V}{6k\Omega} = -2mA$

For  $t \geq 0$ :



$$i(\infty) = 2mA$$

$$\tau = \frac{0.2mH}{4k\Omega} = 50ns$$

$$i(t) = [i(0) - i(\infty)] e^{-t/\tau} + i(\infty)$$

$$= (-4 e^{-2 \times 10^7 t} + 2) \text{ mA}, t \geq 0$$

