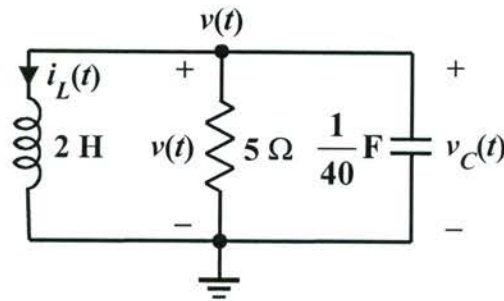


EE 2240  
**Problem #01**

For the underdamped circuit shown, determine the voltage  $v(t)$  if the initial conditions on the storage elements are  $i_L(0) = 1$  A and  $v_C(0) = 10$  V.



From KCL:

$$i_L(0) + \frac{1}{2} \int_0^t v \, dt + \frac{v}{5} + \frac{1}{40} \frac{dv}{dt} = 0 \quad \square$$

Differentiating w.r.t.  $t$ :

$$\frac{1}{2} v + \frac{1}{5} \dot{v} + \frac{1}{40} \ddot{v} = 0 \quad \text{or} \quad \ddot{v} + 8\dot{v} + 20v = 0$$

The characteristic equation is:

$$r^2 + 8r + 20 = 0 \quad \text{or} \quad (r+4)^2 + 2^2 = 0 \Rightarrow r = -4 \pm j2$$

and, therefore,

$$v(t) = e^{-4t} (K_1 \cos 2t + K_2 \sin 2t)$$

From  $\square$  above

$$i_L(0) + \frac{1}{2} \int_0^0 v(t) \, dt + \frac{v(0)}{5} + \frac{1}{40} \dot{v}(0) = 0$$

$$\Rightarrow \dot{v}(0) = -40 i_L(0) - 8 v(0) = -120$$

Solving for  $K_1$  and  $K_2$ , then

$$v(t) = e^{-4t} (10 \cos 2t - 40 \sin 2t)$$

$$= 10 e^{-4t} (\cos 2t - 4 \sin 2t) \text{ V, } t \geq 0$$