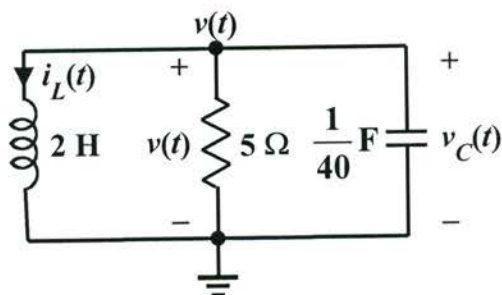


EE 2240
Problem #02

For the underdamped circuit shown, determine the current $i_L(t)$ if the initial conditions on the storage elements are $i_L(0) = 1$ A and $v_C(0) = 10$ V.



From KCL:

$$i_L + \frac{v}{5} + \frac{1}{40} \frac{dv}{dt} = 0 \quad [1]$$

Note that

$$v = 2 \frac{di_L}{dt}, \text{ so that the KCL equation may}$$

be rewritten as:

$$i_L + \frac{2}{5} \frac{di_L}{dt} + \frac{1}{20} \frac{d^2i_L}{dt^2} = 0$$

$$\text{or } \frac{d^2i_L}{dt^2} + 8 \frac{di_L}{dt} + 20i_L = 0$$

The corresponding characteristic equation is:

$$r^2 + 8r + 20 = 0 \text{ or } r = -4 \pm j2$$

$$\text{Therefore, } i_L(t) = e^{-4t} (K_1 \cos 2t + K_2 \sin 2t)$$

$$\text{From [1], } \left. \frac{di_L}{dt} \right|_{t=0} = \frac{1}{2} v(0) = 5$$

Solving for K_1 and K_2 , we have

$$i_L(t) = e^{-4t} \left(\cos 2t + \frac{9}{2} \sin 2t \right) \text{ A, } t \geq 0$$