

EE 2240
Problem #06

The switch has been closed for a *very* long time. It is opened at $t = 0$. Find $v(t)$ for $t \geq 0$.

