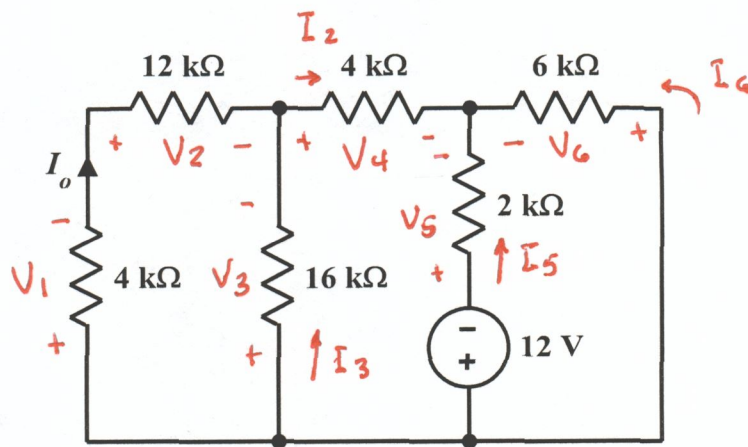


EE 2240  
**Problem #09**

Determine the value of  $I_o$ .



$$V_1 = (4k\Omega) I_o$$

$$V_2 = (12k\Omega) I_o$$

$$V_3 = V_1 + V_2 = 16000 I_o$$

$$I_3 = \frac{V_3}{16k\Omega} = I_o$$

$$I_2 = I_o + I_3 = 2I_o$$

$$V_4 = (4k\Omega) I_2 = 8000 I_o$$

$$V_5 = -12 + V_3 + V_4 = -12 + 24000 I_o$$

$$I_5 = \frac{V_5}{2k\Omega} = -6mA + 12 I_o$$

$$I_6 = -I_2 - I_5 = 6mA - 14 I_o$$

$$V_6 = (6k\Omega) I_6 = 36V - 84000 I_o$$

$$V_6 - V_5 = 12V \Rightarrow 48 - 108000 I_o = 12$$

$$I_o = \frac{48 - 12}{108000} = \frac{1}{3} mA$$