

EE 2240  
**Problem #02**

Use a sequence of source transformations and equivalent resistance calculations to determine  $V_x$  in the circuit shown below.

