
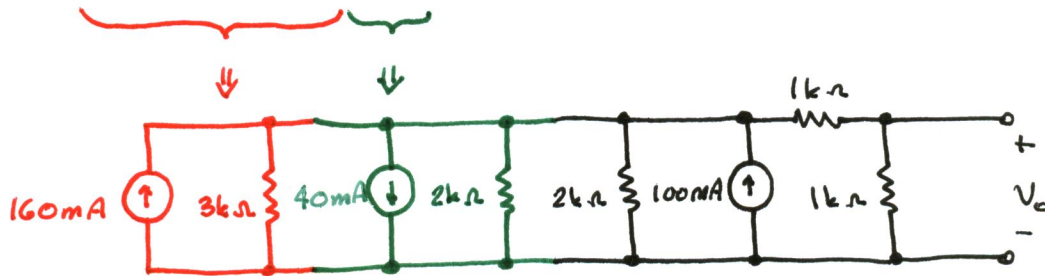




EE 2240
Problem #04

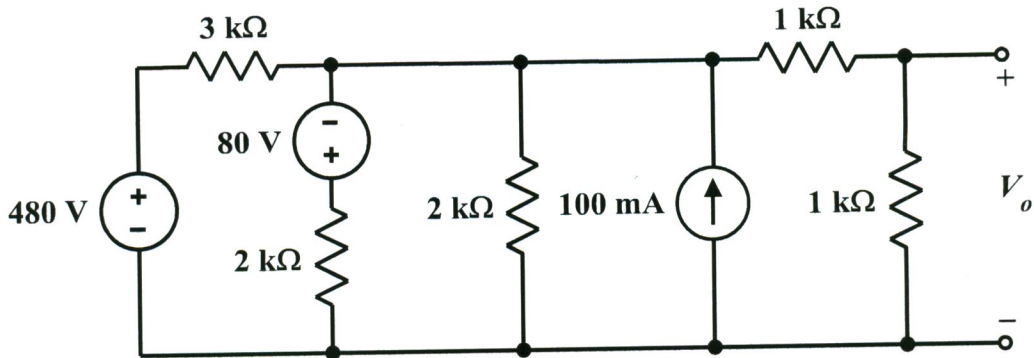Find V_o using a sequence of source transformations.



$$160\text{mA} - 40\text{mA} + 100\text{mA} = 220\text{mA}$$
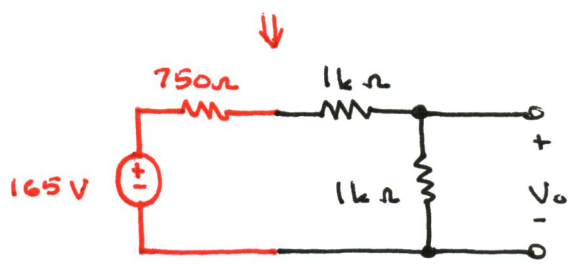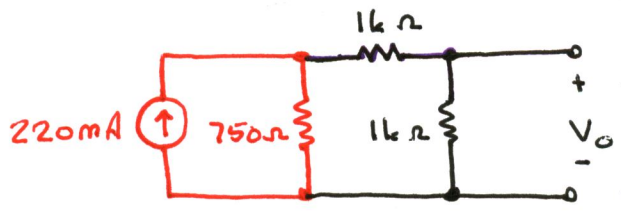
$$3\text{k}\Omega \parallel 2\text{k}\Omega \parallel 1\text{k}\Omega = 750\Omega$$



$$V_o = \frac{1\text{k}\Omega}{750\Omega + 1\text{k}\Omega + 1\text{k}\Omega} (165\text{V})$$

$$= 60\text{V}$$