

EE 2240
Problem #05

Use a sequence of source transformations to determine the value of V_y . Show all of your work.

