

EE 2240  
**Problem #02**

Use superposition to find  $I_o$ . Show the details of your work.

