

EE 2240
Problem #04

Use the superposition method to find I , and then calculate the power dissipated in the 900Ω resistor.

