
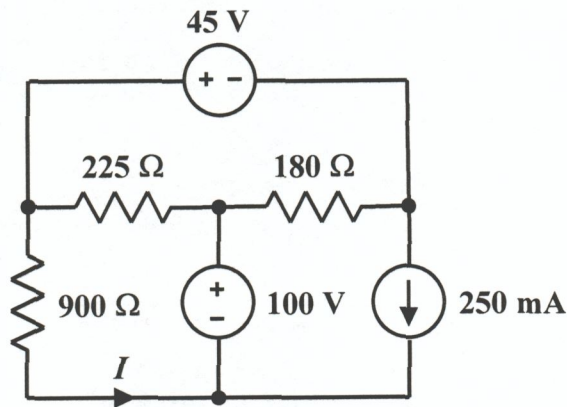


EE 2240
Problem #04

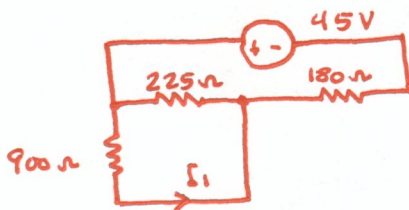Use the superposition method to find I , and then calculate the power dissipated in the 900Ω resistor.




For the 45V source:



$$225\Omega \parallel 900\Omega = 180\Omega$$

$$I_1 = \frac{\frac{1}{2}(45V)}{900\Omega} = 25\text{ mA}$$


For the 100V source:

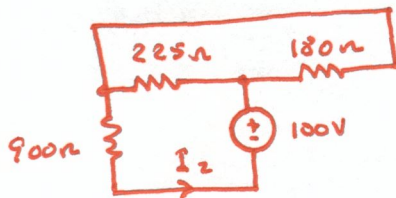

$$225\Omega \parallel 180\Omega = 100\Omega$$

$$I_2 = \frac{\frac{9}{10}(100V)}{900\Omega} = 100\text{ mA}$$

For the 250mA source:

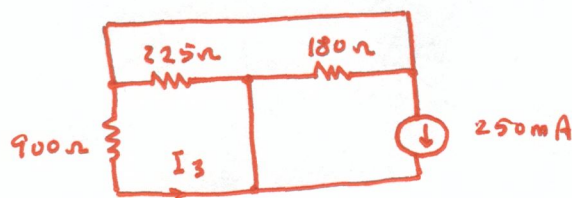

$$I_3 = - \frac{\frac{1}{900}}{\frac{1}{900} + \frac{1}{225} + \frac{1}{180}} (250\text{ mA}) = -25\text{ mA}$$

$$I = I_1 + I_2 + I_3 = 25 + 100 - 25 = 100\text{ mA}$$

$$P_{900\Omega} = I^2(900\Omega) = 9\text{ W}$$