

EE 2240  
**Problem #05**

Treat the  $2\text{k}\Omega$  resistor as the load, and use Thévenin's Theorem to determine  $V_x$ .

