

EE 4474/5574

Homework Problem #007

X and Y are linear components. If $I_0 = 20$ mA when $V_S = 125$ V, what will be the new value of I_0 if V_S is increased to 200 V?

