

EE 4474/5574

**Homework Problem #13**

For the circuit of Problems 11 and 12, determine the resulting *driving point (input) impedance* if a  $20\ \Omega$  resistor is connected between the output terminals. Express the result in polar form.