

EE 4474/5574

Homework Problem #017

Synthesize a passive network whose input impedance is

$$Z(s) = 16 + \frac{9s}{4 + 3s}$$