

EE 4474/5574

**Homework Problem #018**

Synthesize a passive network whose input impedance is

$$Z(s) = \frac{2s^4 + 8s^2 + 6}{s^3 + 2s}$$