

EE 4474/5574

**Homework Problem #019**

Synthesize a passive network whose input impedance is

$$Z(s) = \frac{s^5 + 3s^3 + 2s}{2s^6 + 11s^4 + 16s^2 + 4}$$