

EE 4474/5574

**Homework Problem #020**

Synthesize the following expression as both an impedance and an admittance:

$$F(s) = \frac{8(s+4)(s+2)}{(s+3)(s+10)}$$