

EE 4474/5574

Homework Problem #021

Synthesize the following expression as a *voltage transfer function*:

$$H(s) = \frac{1}{s+2}$$